

Solutions to Exercises

Chapter 1

Exercise 1. Use Eq. (1.6) and take the resistivity value from Table 1.2. Also, the wire has diameter $1 \text{ mm} = 10^{-3} \text{ m}$ so the area is $A = \pi r^2 = \pi \left(\frac{10^{-3} \text{ m}}{2}\right)^2 = 7.85 \times 10^{-3} \text{ m}^2$. Finally, the length of the wire is 1 m , so $R = \rho \frac{L}{A} = (100 \times 10^{-8} \Omega \cdot \text{m}) \left(\frac{1 \text{ m}}{7.85 \times 10^{-3} \text{ m}^2}\right) = 1.27 \Omega$.

Exercise 2. Equation (1.7) gives $P = I^2 R$ for resistors. Thus $I_{max} = \sqrt{P/R}$. For the 10 W resistor we obtain $I_{max} = \sqrt{(10 \text{ W}/10 \text{ k}\Omega)} = 0.032 \text{ A}$ and for the quarter-watt resistor $I_{max} = \sqrt{(0.25 \text{ W}/10 \text{ k}\Omega)} = 0.005 \text{ A}$.

Exercise 3. Equation (1.8) gives $P = V^2/R$ for resistors. For the 100Ω resistor we obtain $P = (100 \text{ V})^2/100 \Omega = 100 \text{ W}$ while for the $100 \text{ k}\Omega$ resistor we obtain $P = (100 \text{ V})^2/100 \text{ k}\Omega = 0.1 \text{ W}$.

Exercise 4. The current through R_3 is the same as the current supplied by the battery. To find this current, we first find the total resistance of the circuit. The parallel combination of R_1 and R_2 is $\frac{R_1 R_2}{R_1 + R_2} = \frac{6 \cdot 5}{6 + 5} = 2.73 \Omega$. This resistance is then in series with R_3 so $R_{tot} = 3 \Omega + 2.73 \Omega = 5.73 \Omega$ and $I_3 = V_1/R_{tot} = 5 \text{ V}/5.73 \Omega = 0.873 \text{ A}$.

Exercise 5. Building on the result of the previous problem, the voltage across R_1 and R_2 is $V_1 - I_3 R_3 = 5 \text{ V} - (0.873 \text{ A})(3 \Omega) = 2.38 \text{ V}$. Therefore, $I_2 = (2.38 \text{ V})/(6 \Omega) = 0.397 \text{ A}$ and $I_1 = (2.38 \text{ V})/(5 \Omega) = 0.476 \text{ A}$.

Exercise 6. When the meter is connected, the input resistance of the meter R_m will be in parallel with the $1 \text{ k}\Omega$ resistor (call this resistor R_2). The resulting circuit will still be a voltage divider, but R_2 is replaced by the parallel combination of R_2 and R_m , $R_2//R_m = \frac{R_2 R_m}{R_2 + R_m}$. The voltage across this resistance is then given by the voltage divider equation [Eq. (1.21)]:

$$V_{out} = V_{in} \frac{R_2//R_m}{R_1 + (R_2//R_m)} = V_{in} \frac{R_2 R_m}{R_1 R_2 + R_1 R_m + R_2 R_m}$$

where we have called the $2 \text{ k}\Omega$ resistor R_1 . Putting in the numbers:


$$R_m = 100 \Omega : V_{out} = 3 \text{ V} \frac{(1 \text{ k}\Omega)(100 \Omega)}{(2 \text{ k}\Omega)(1 \text{ k}\Omega) + (2 \text{ k}\Omega)(100 \Omega) + (1 \text{ k}\Omega)(100 \Omega)} = 0.130 \text{ V}$$

$$R_m = 1 \text{ k}\Omega : V_{out} = 3 \text{ V} \frac{(1 \text{ k}\Omega)(1 \text{ k}\Omega)}{(2 \text{ k}\Omega)(1 \text{ k}\Omega) + (2 \text{ k}\Omega)(1 \text{ k}\Omega) + (1 \text{ k}\Omega)(1 \text{ k}\Omega)} = 0.600 \text{ V}$$

$$R_m = 50 \text{ k}\Omega : V_{\text{out}} = 3 \text{ V} \frac{(1 \text{ k}\Omega)(50 \text{ k}\Omega)}{(2 \text{ k}\Omega)(1 \text{ k}\Omega) + (2 \text{ k}\Omega)(50 \text{ k}\Omega) + (1 \text{ k}\Omega)(50 \text{ k}\Omega)} = 0.987 \text{ V}$$

$$R_m = 1 \text{ M}\Omega : V_{\text{out}} = 3 \text{ V} \frac{(1 \text{ k}\Omega)(1 \text{ M}\Omega)}{(2 \text{ k}\Omega)(1 \text{ k}\Omega) + (2 \text{ k}\Omega)(1 \text{ M}\Omega) + (1 \text{ k}\Omega)(1 \text{ M}\Omega)} = 0.999 \text{ V}$$

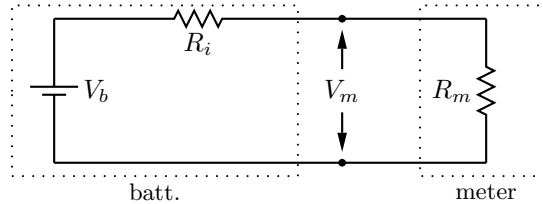Exercise 7. When the voltmeter is attached the circuit appears as shown below.




This is a voltage divider so $V_m = V_b \frac{R_m}{R_i + R_m}$. Solving for R_i gives $R_i = R_m \frac{V_b}{V_m} - R_m = (1000 \Omega) \frac{1.5 \text{ V}}{0.9 \text{ V}} - 1000 \Omega = 667 \Omega$.

Exercise 8. Referring to the diagram for Exercise 7, we have $V_m = V_b \frac{R_m}{R_m + R_i} = (1.5 \text{ V}) \frac{1 \text{ M}\Omega}{1 \text{ M}\Omega + 667 \Omega} = 1.499 \text{ V}$.

Exercise 9. Start by combining the 10Ω and 5Ω resistors in series to form a 15Ω resistor. This, in parallel with the existing 15Ω resistor gives a 7.5Ω resistor. This resistor is in series with the 3Ω and 2Ω , giving a total of $3 + 7.5 + 2 = 12.5 \Omega$ across the terminals.

Exercise 10. From the result of Exercise 9 we know that the current supplied by the battery is $I_1 = V_{\text{bat}}/R_{\text{tot}} = 25 \text{ V}/12.5 \Omega = 2 \text{ A}$. This means the voltage across the 15Ω resistor is $V_{15} = 25 \text{ V} - I_1(3 \Omega + 2 \Omega) = 15 \text{ V}$. This is also the voltage across the series combination of the 10Ω and 5Ω resistors. Thus the current through the 10Ω resistor is $V_{15}/(10 \Omega + 5 \Omega) = 1 \text{ A}$.

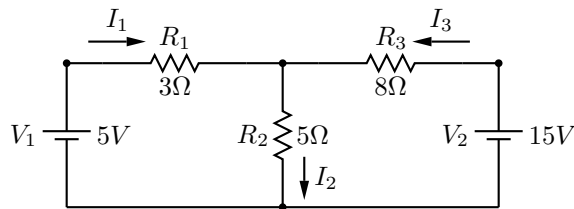Exercise 11. Assign current names and directions as shown below. For the left and right



halves of the circuit, KVL gives

$$\text{a) } V_1 - I_1 R_1 - I_2 R_2 = 0$$

$$\text{b) } V_2 - I_3 R_3 - I_2 R_2 = 0 \rightarrow I_3 = \frac{V_2 - I_2 R_2}{R_3}$$

and KCL gives $I_1 + I_3 = I_2$ or $I_1 = I_2 - I_3$. Using this last result in a) gives

$$V_1 - (I_2 - I_3)R_1 - I_2 R_2 = 0$$